

Lab 7

By Gabby Vargas Leon

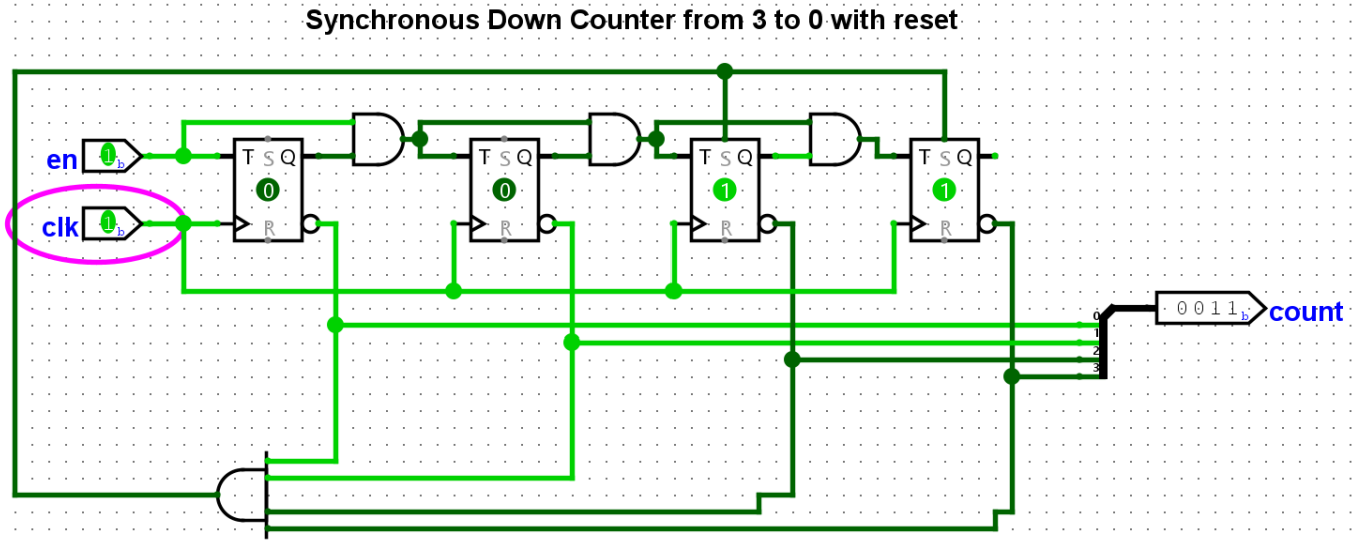
Fixing count down from 10 thru 0 to 3 thru 0




My design for FSM

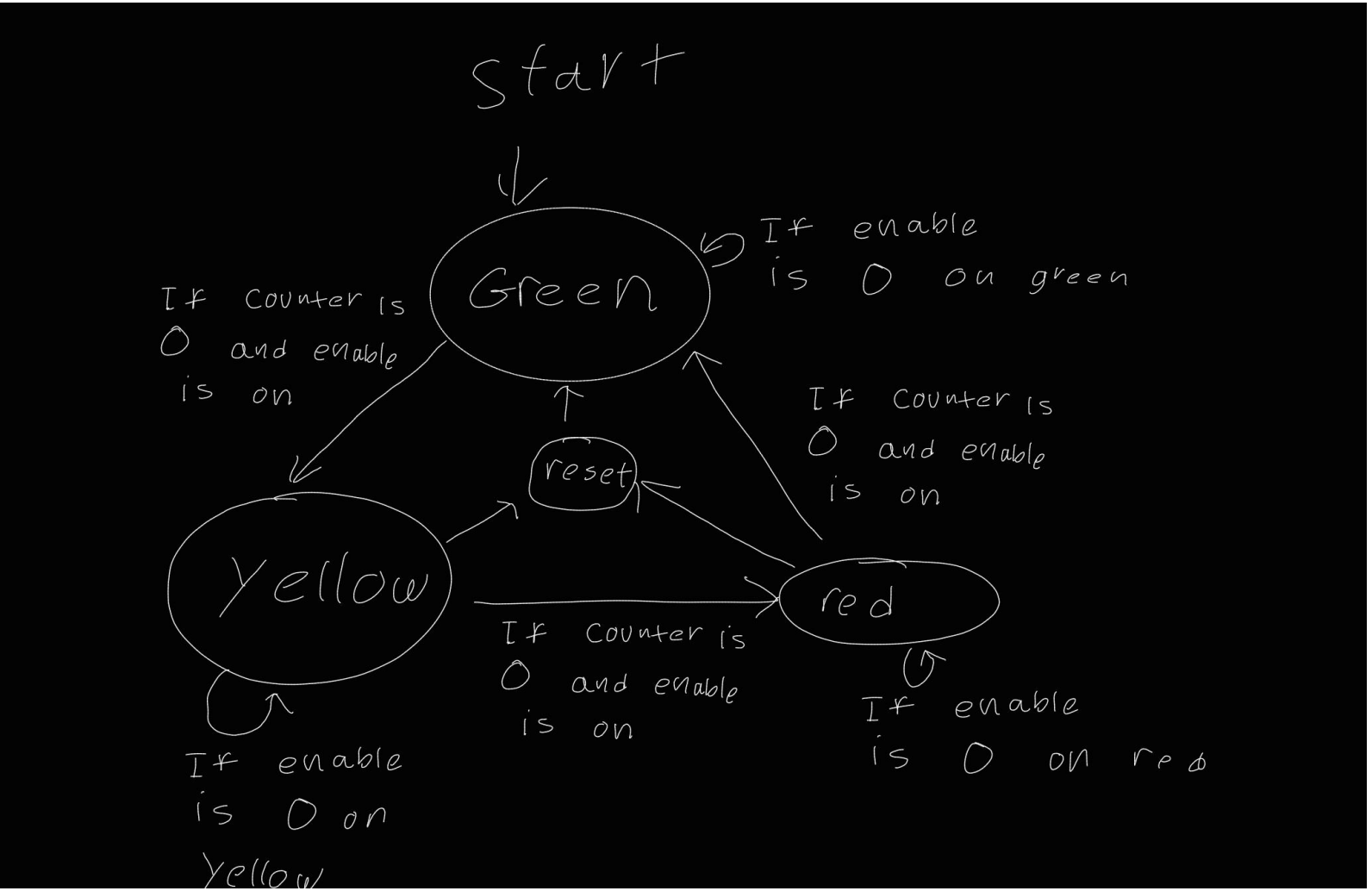


FSM design from the whiteboard

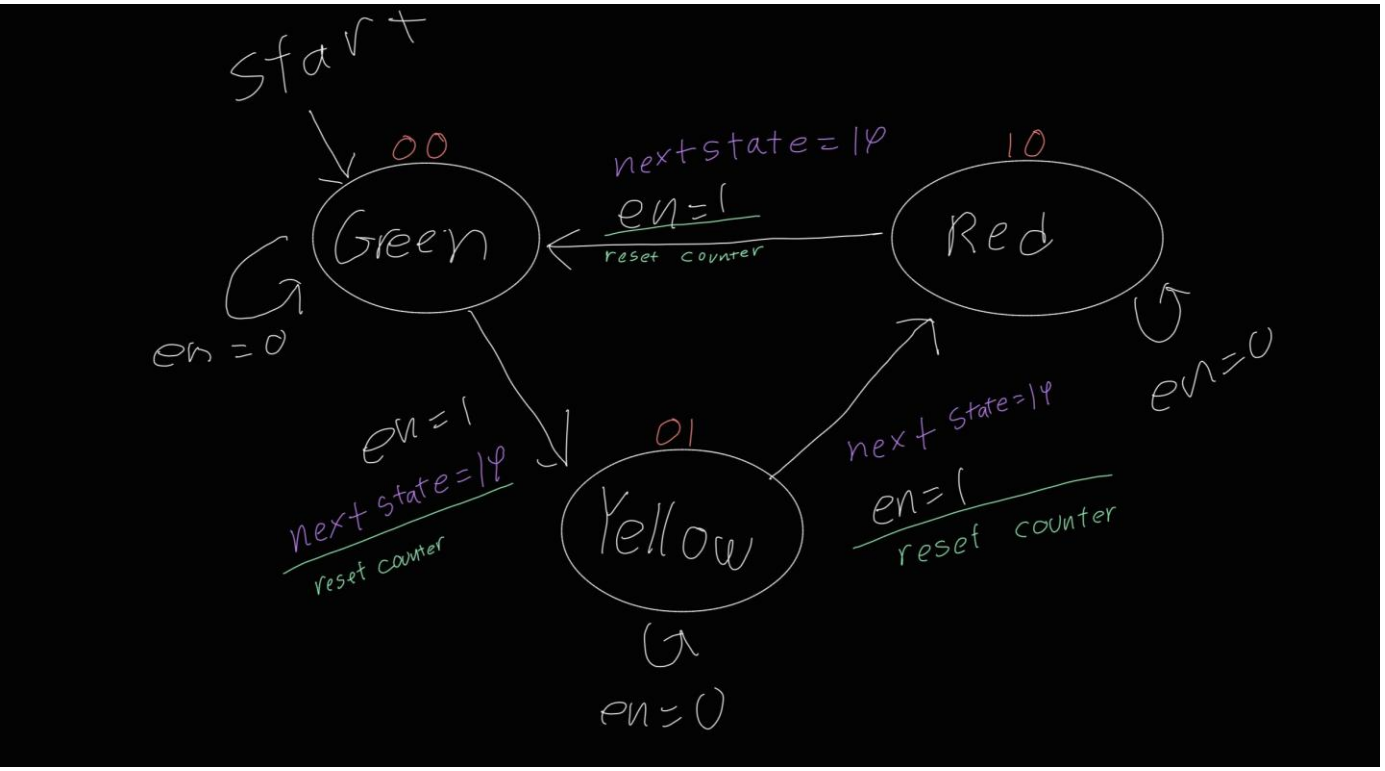


Comparing the two designs

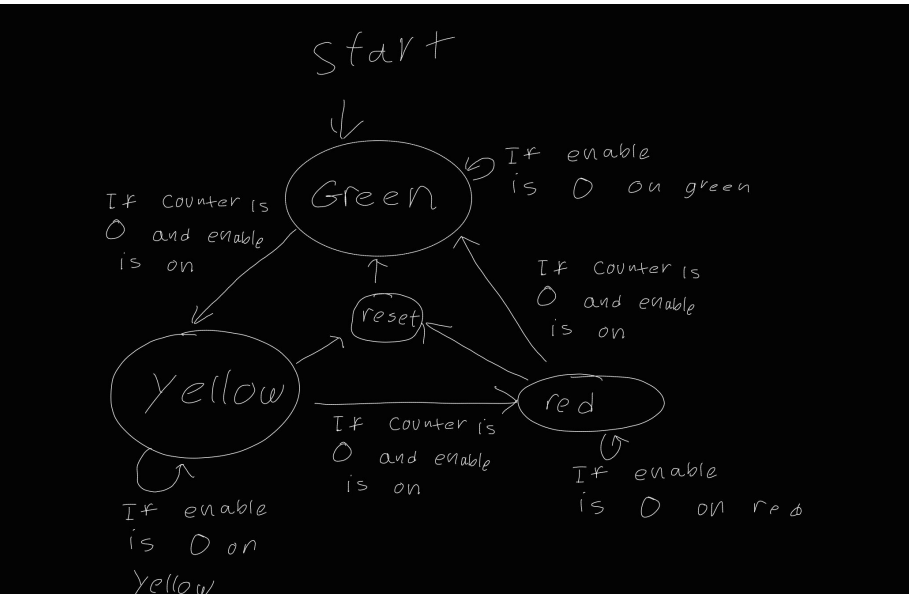

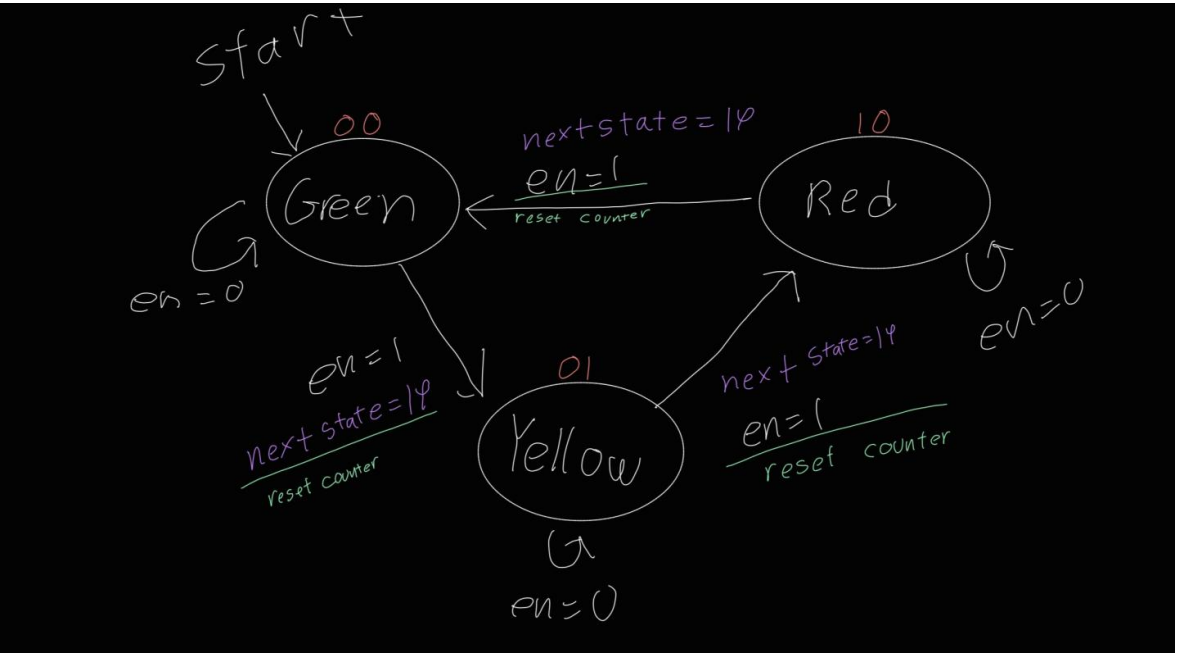


The one done in the white board is less word to state the same things that I write and unnecessary didn't really need the reset state to go back to green

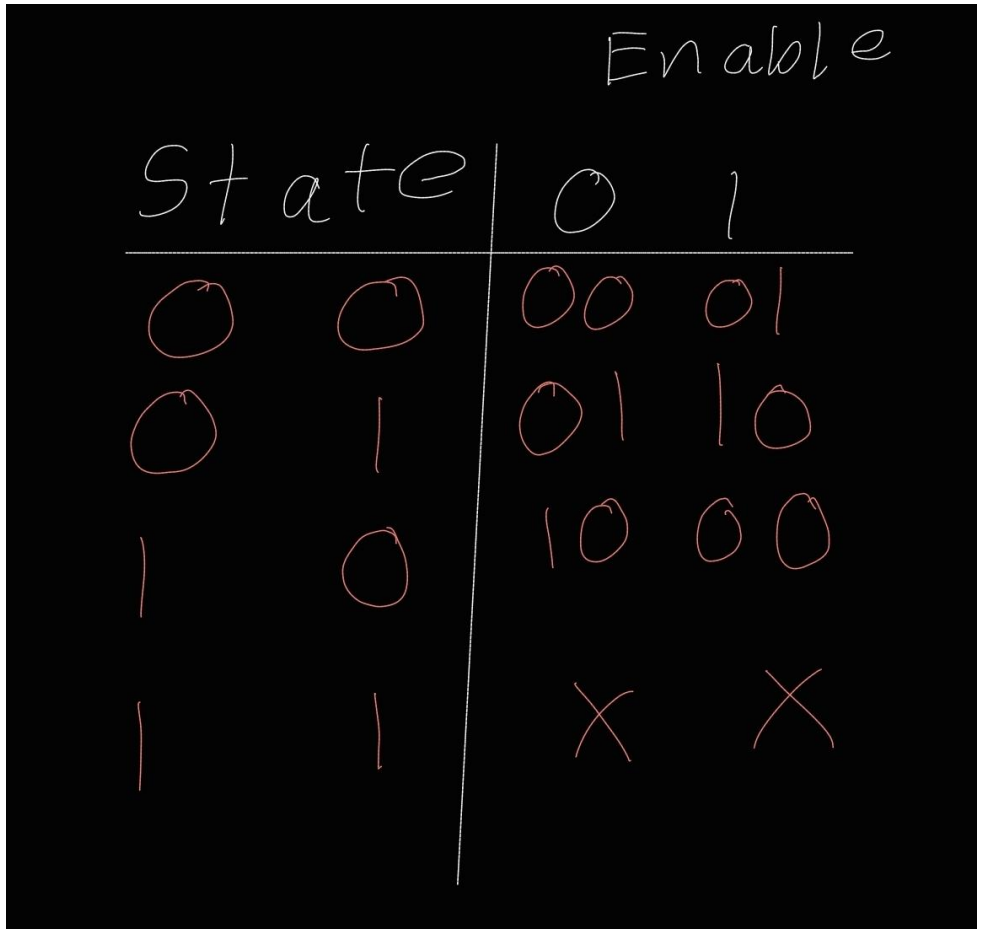
Truth table for the multiplexer that was done in class



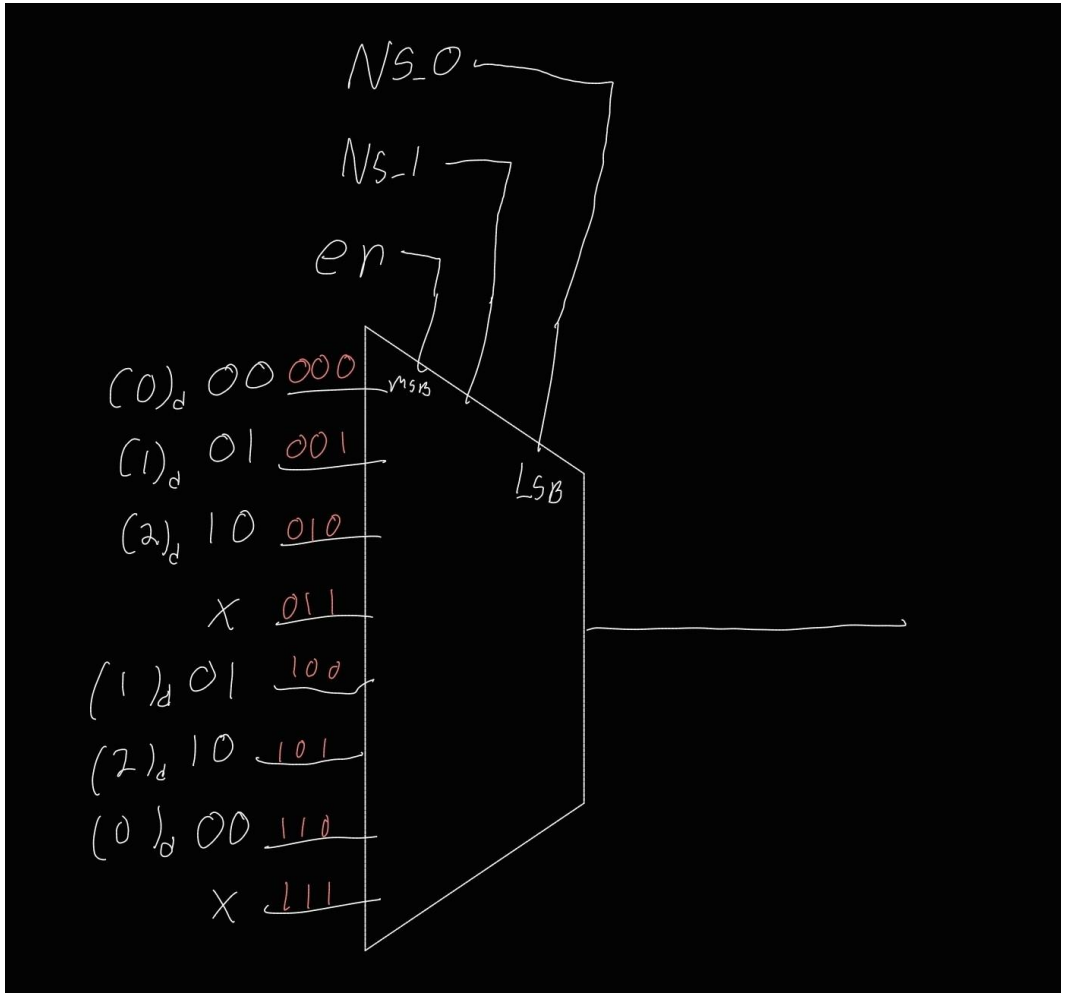
Multiplexer design that was done in class



FSM circuit in Logisim

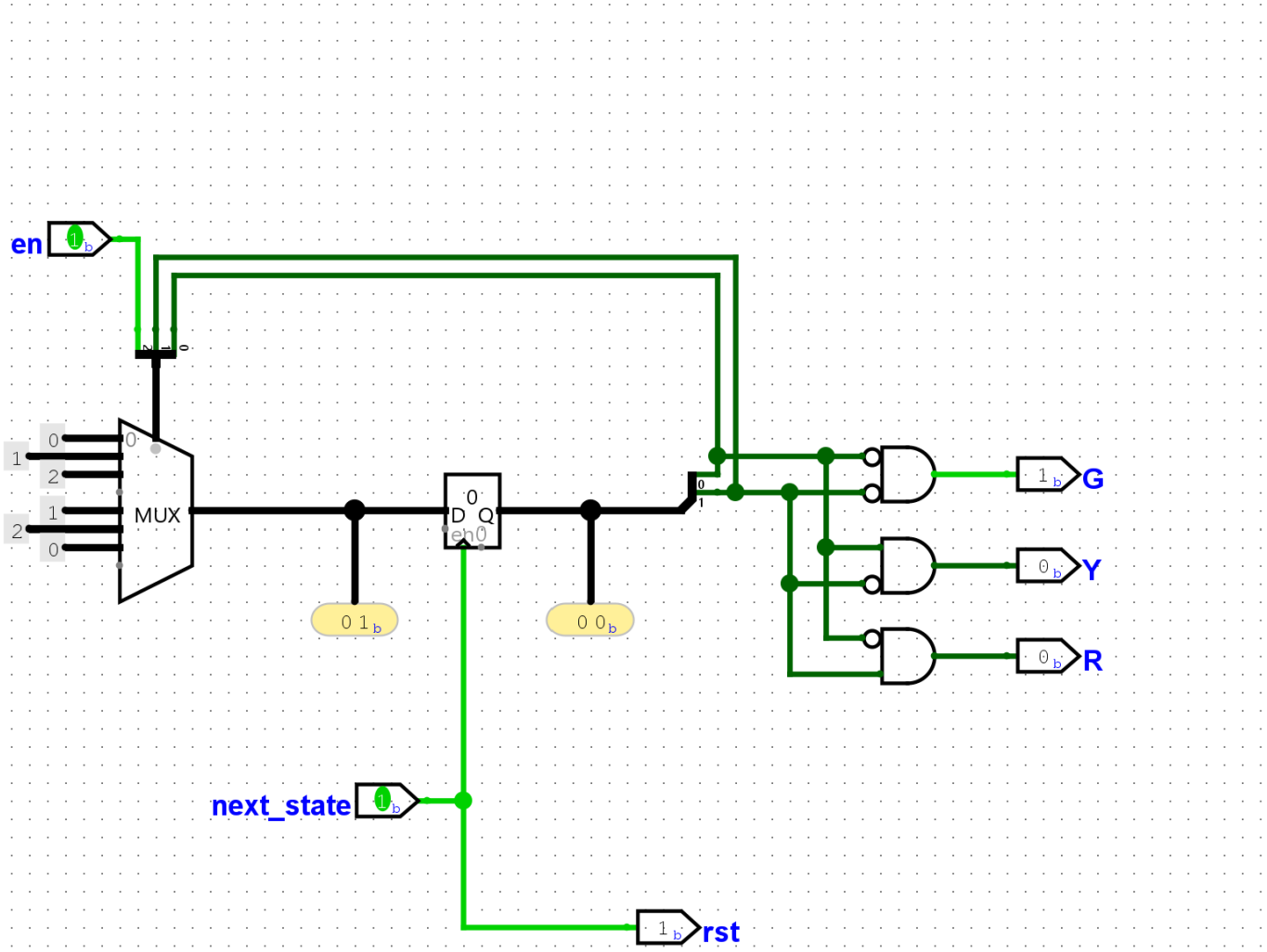

The final circuit

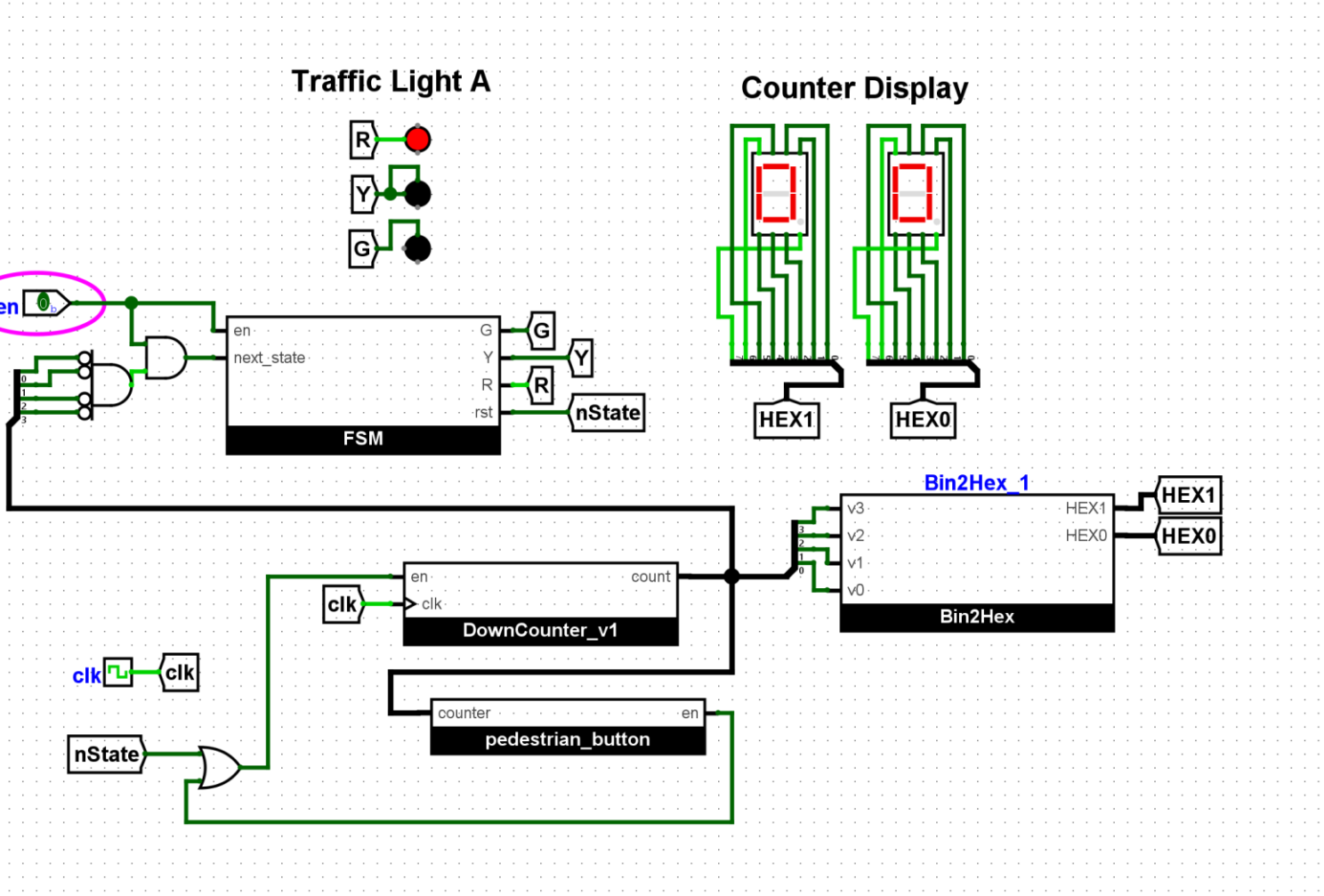

When the counter Display reaches zero it would turn on the next LED in the row and reset the counter display back to 3 and repeat that