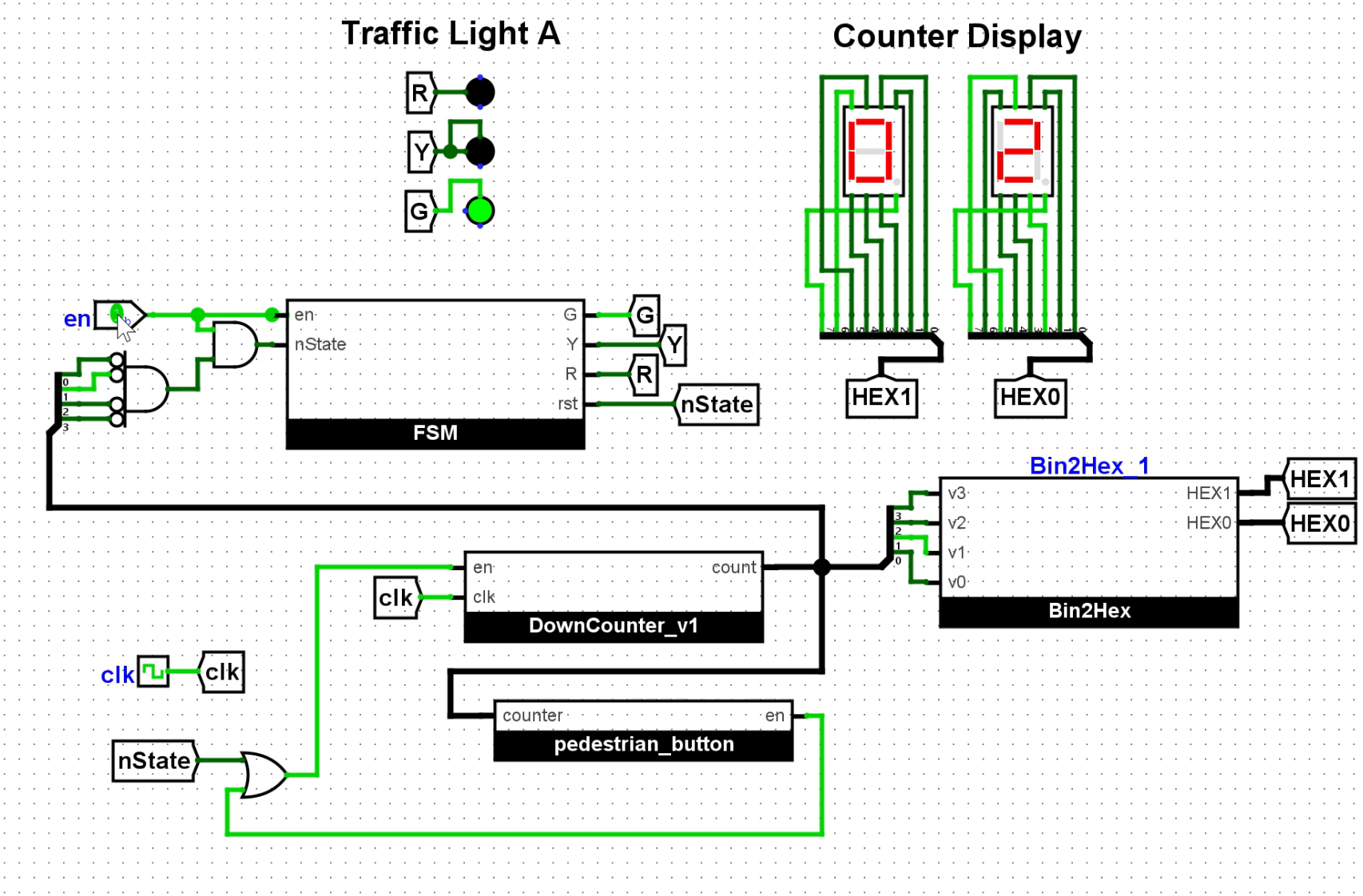
Traffic Light

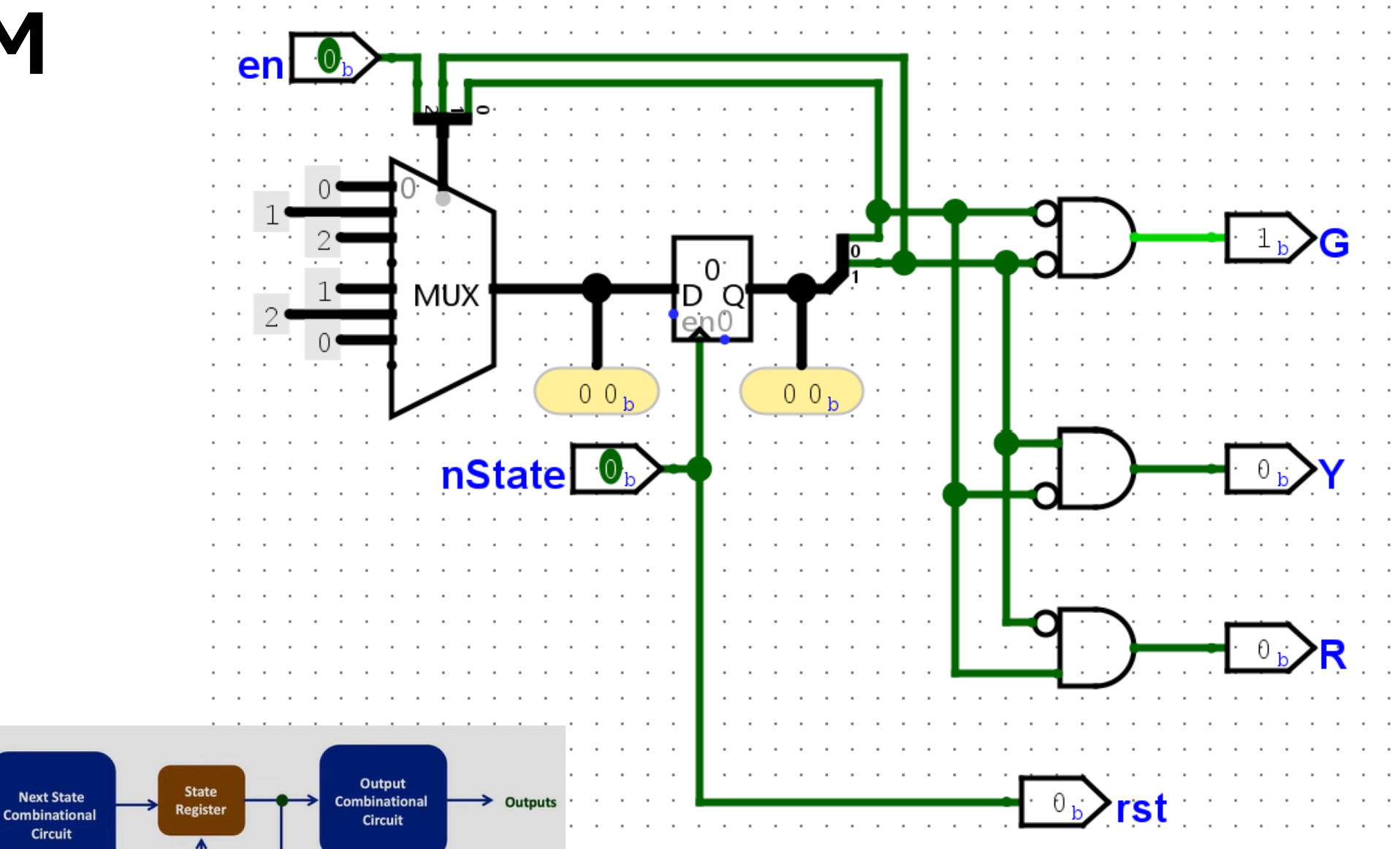


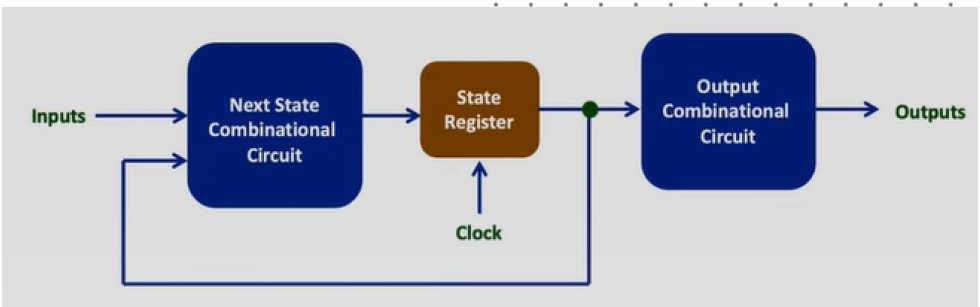
Steps

1. Fix “DownCounter_v1” to count from 3 to 0
2. Design the FSM to cycle between Green, Yellow, Red traffic lights
3. Implement the FSM in Logisim
4. Connect the FSM to the rest of the circuit

Templates

FSM


en
0 b
MUX
0
1
2
0
1
2
0
D Q
en
0 0 b
0 0 b
nState
0 b
1 b
G
0 b
Y
0 b
R
0 b
rst


Inputs
Next State Combinational Circuit
State Register
Clock
Output Combinational Circuit
Outputs