

Lab 8

By Gabby Vargas Leon

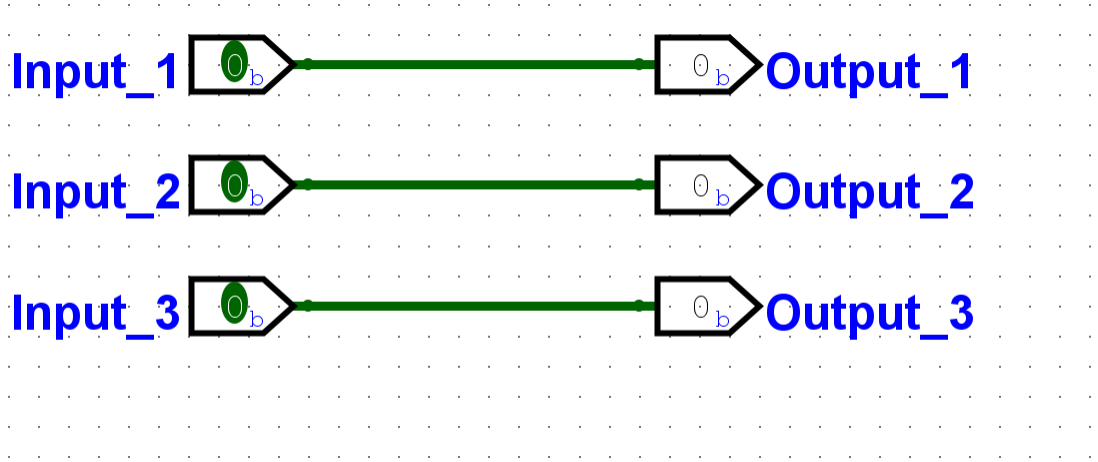Trying to make the RGB LED to work with different inputs on



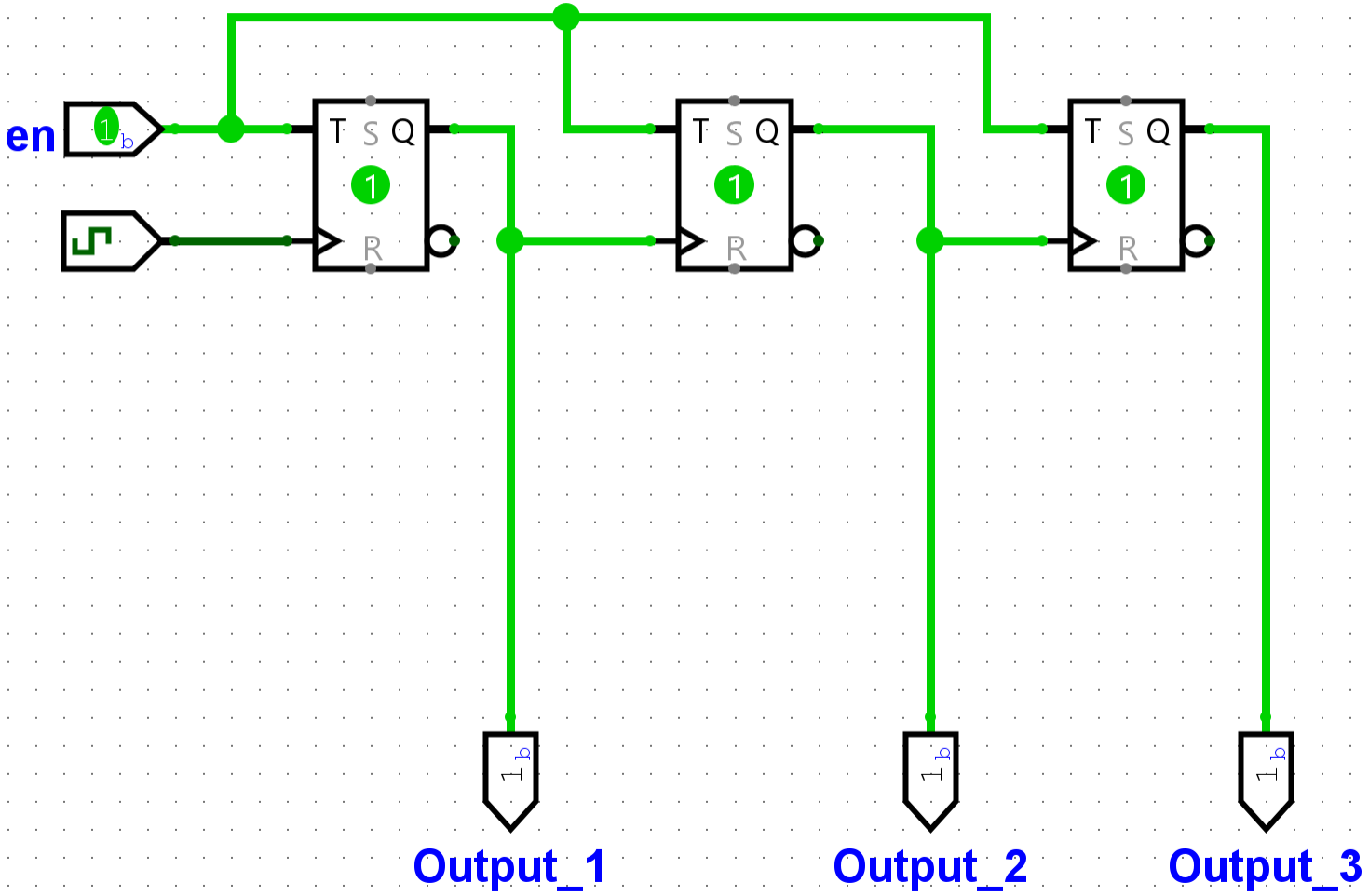Circuit that cycle 8 different patterans at 1 sec rate with a down counter



Circuit that cycle 8 different patterns at 1 sec rate with a down counter that blinks red or green

