

# Final Lab

By Gabby Vargas Leon


# My second FSM

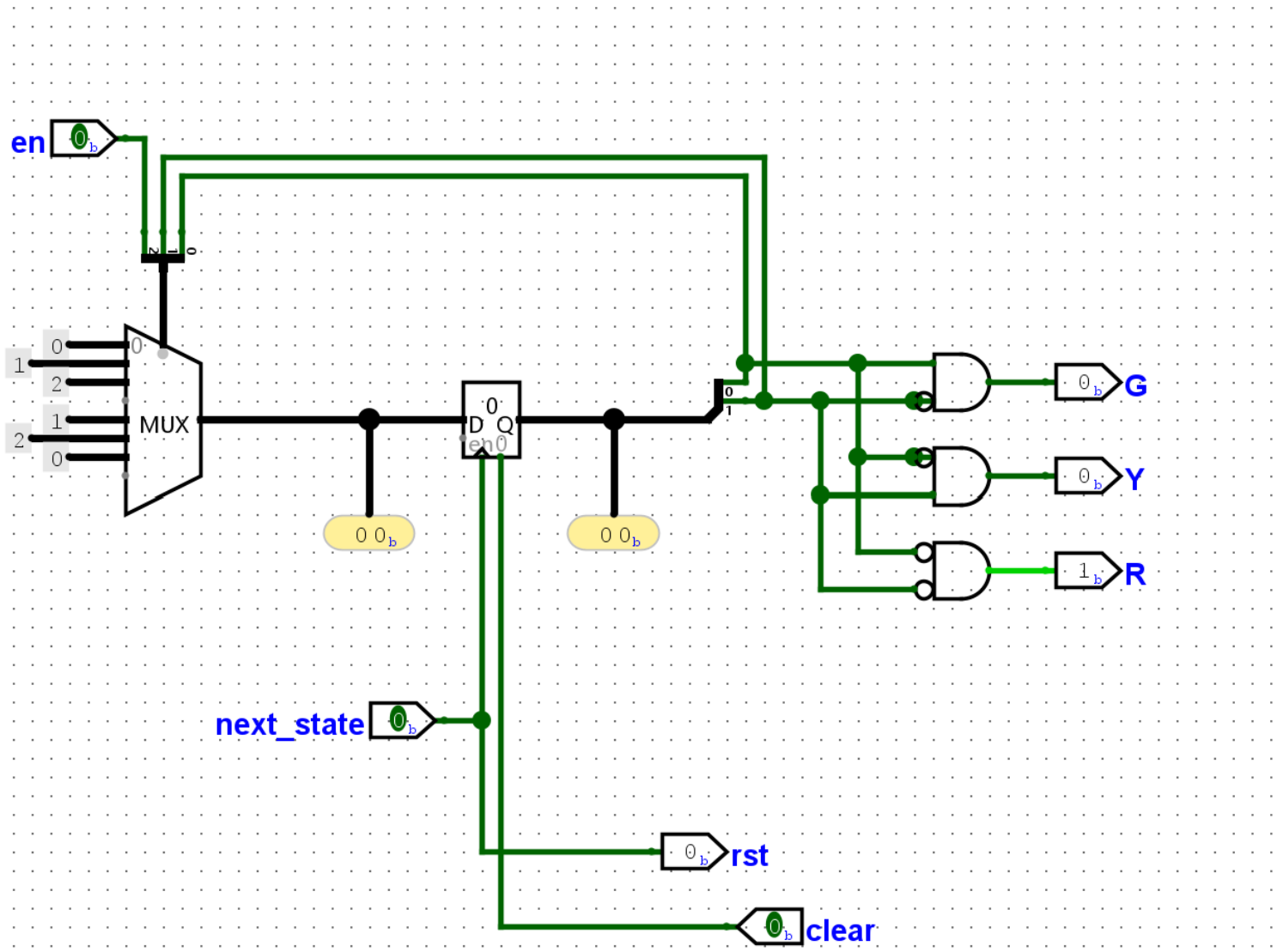


# My First FSM

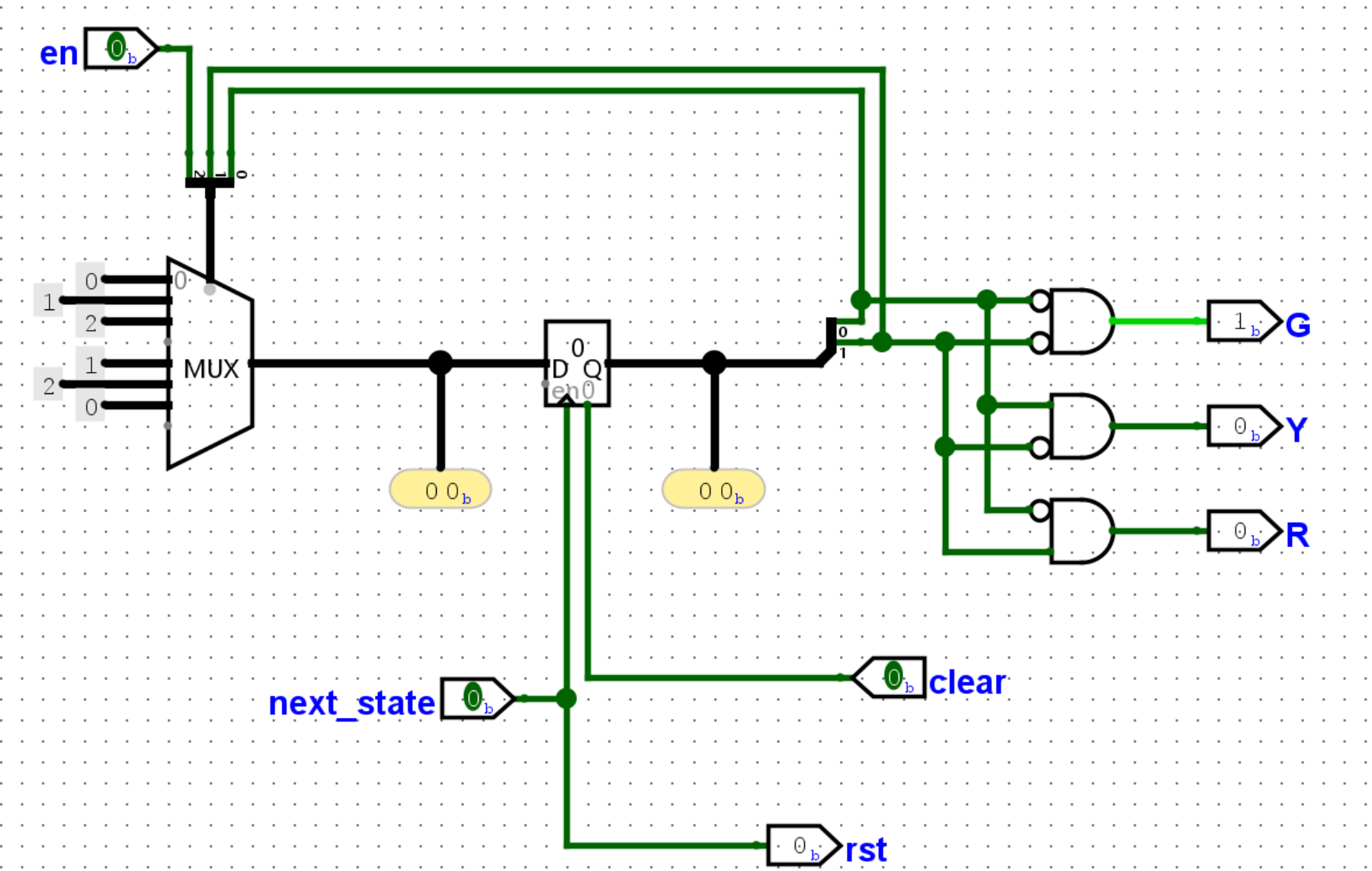


# My pedestrian count down from 10 to 0

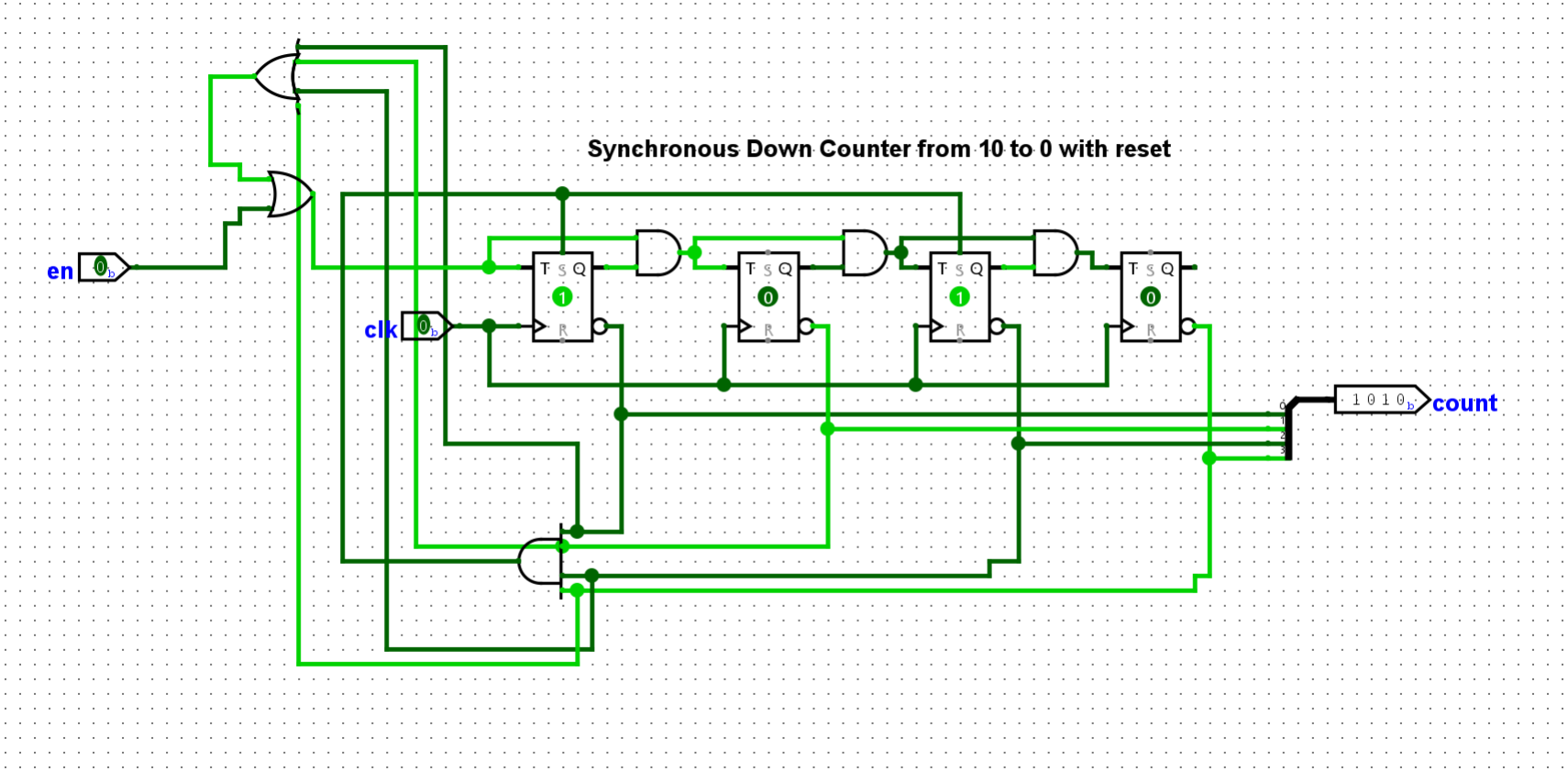
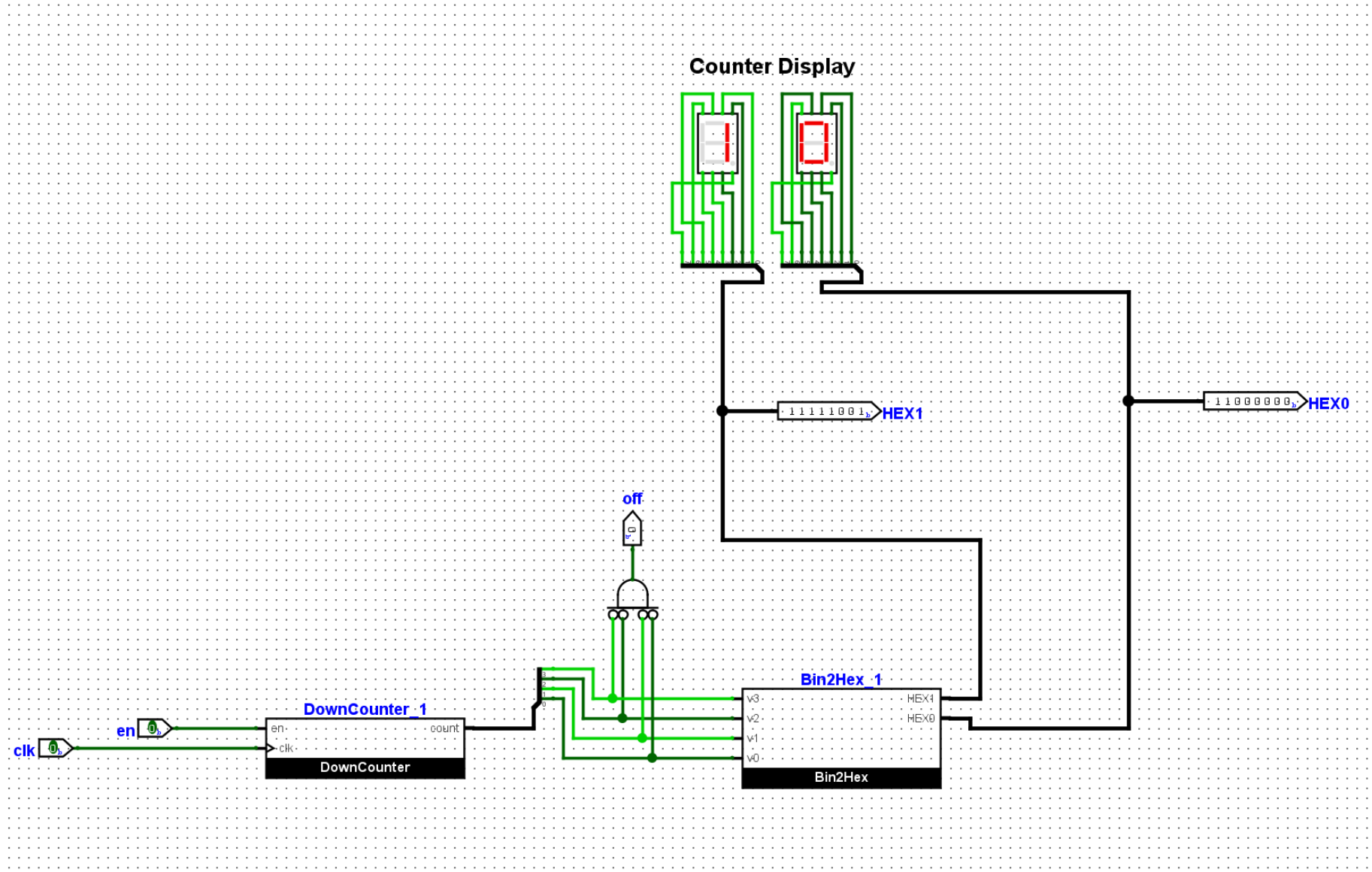
# 10 to 0 countdown with a display showing the number




# Got the traffic light to rotate

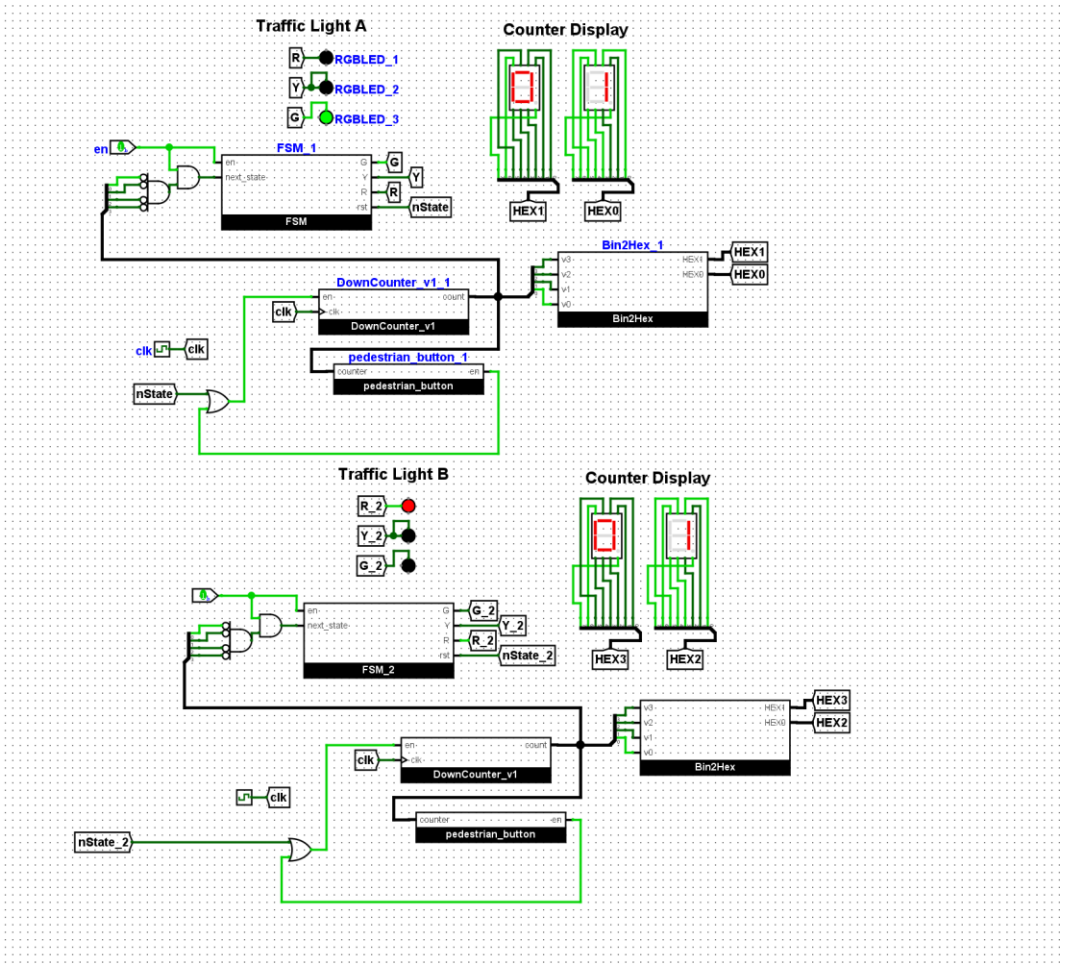


# Made a circuit for both my FSM and FSM2 that that have the display


FSM 1

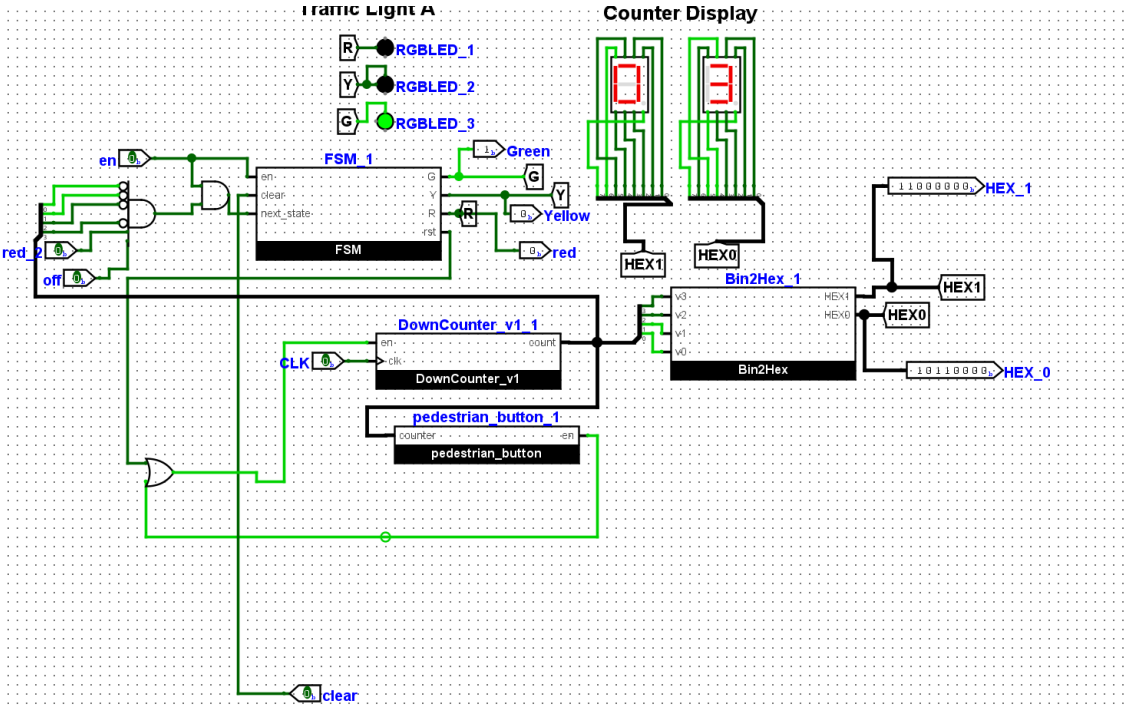


FSM 2

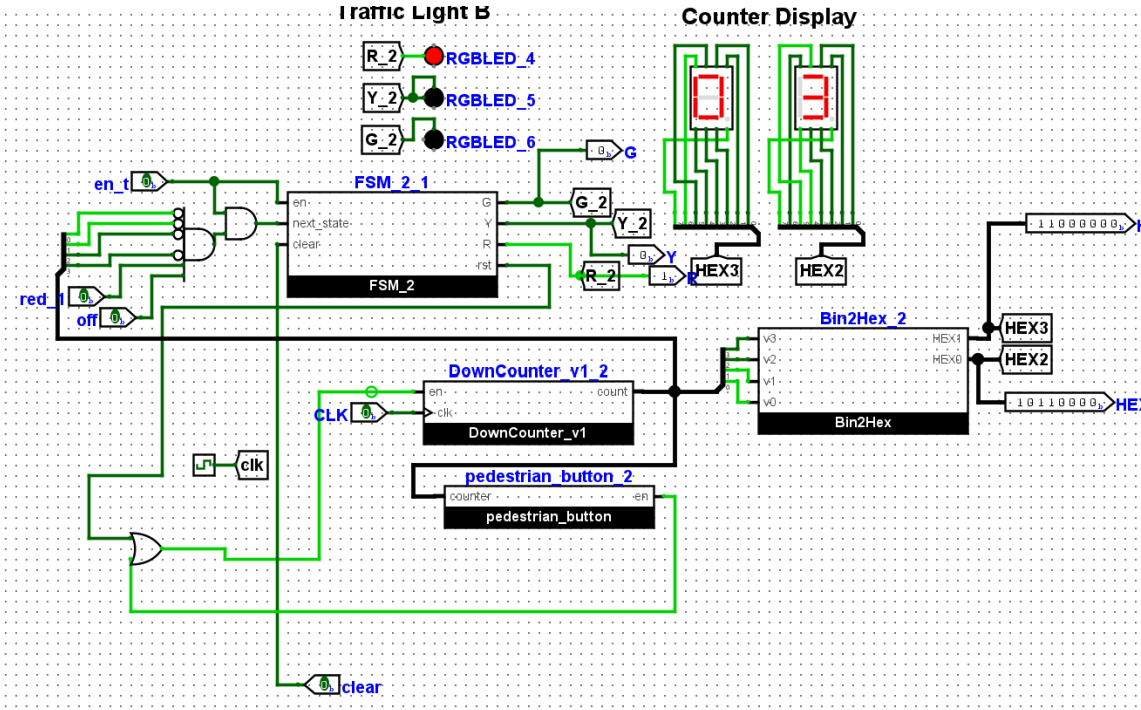


# Walkway button

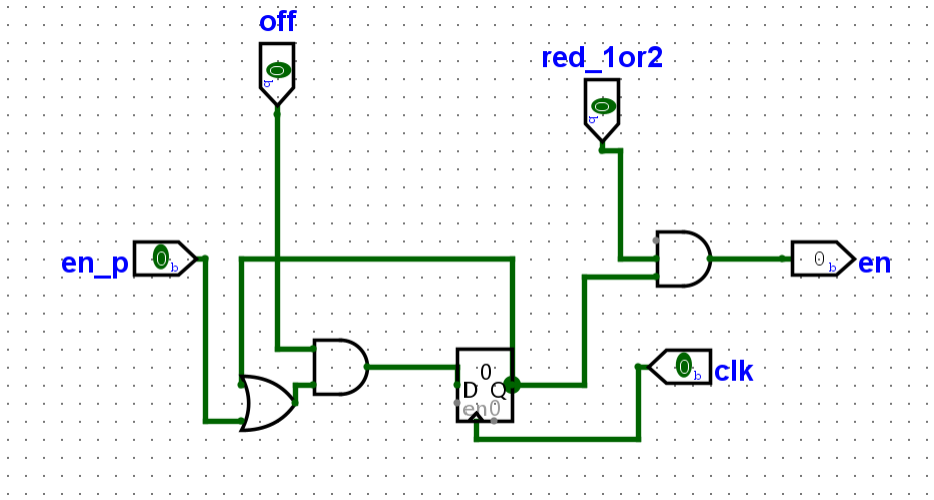



A circuit that remembers that the button was pushed by someone, so they don’t have to hold the button down
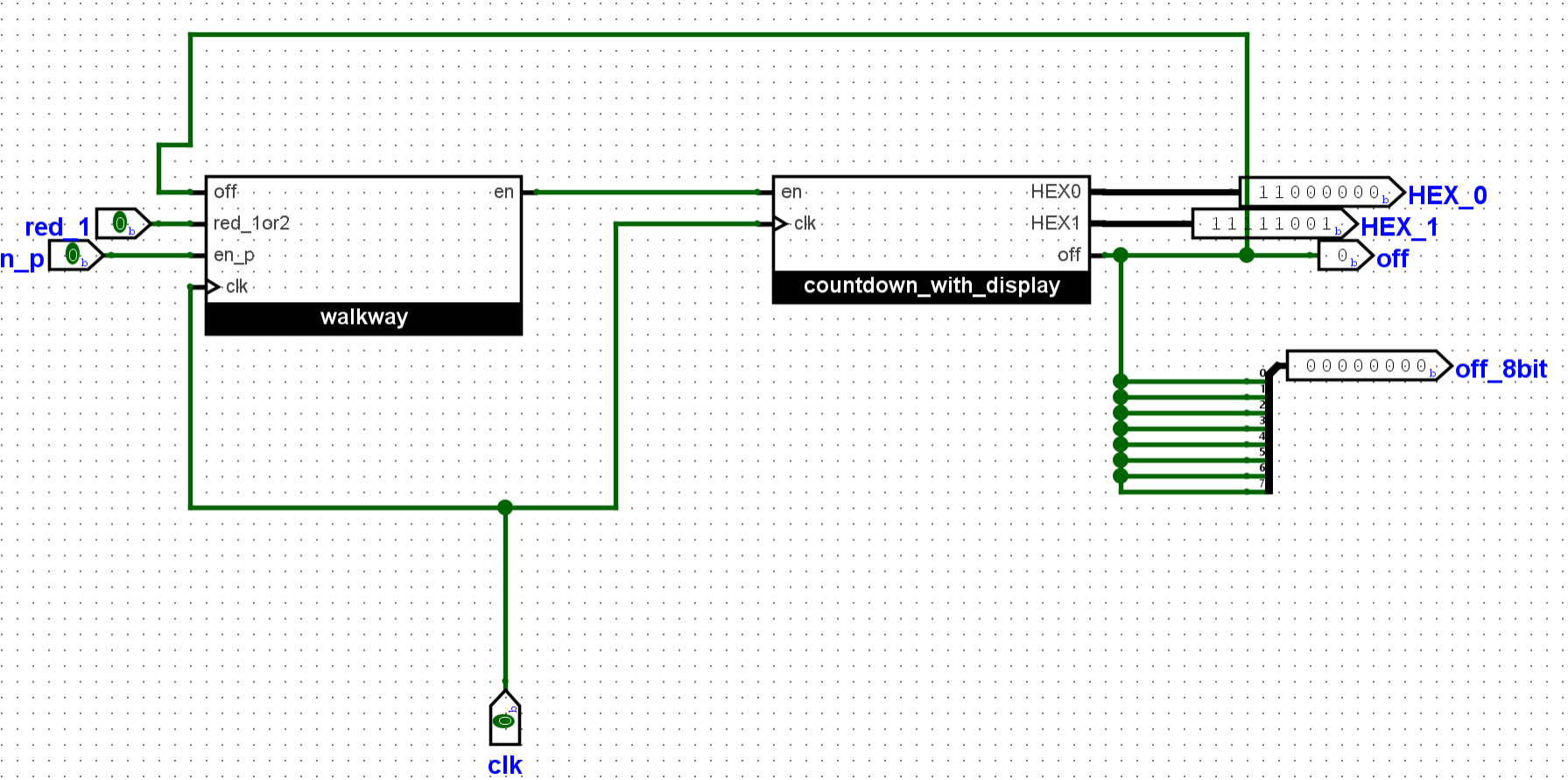
# My walkway circuit that connects to my countdown with display




# Display circuit

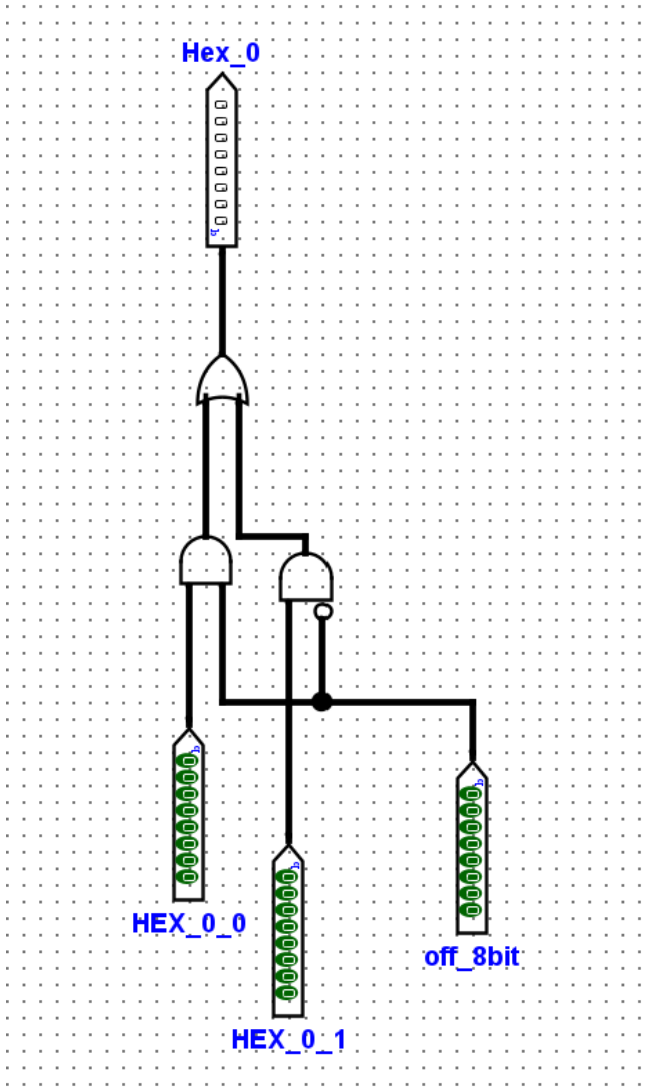



I made a display circuit so that I don’t have to make the same circuit for all my circuit designs


# The count for the first FSM

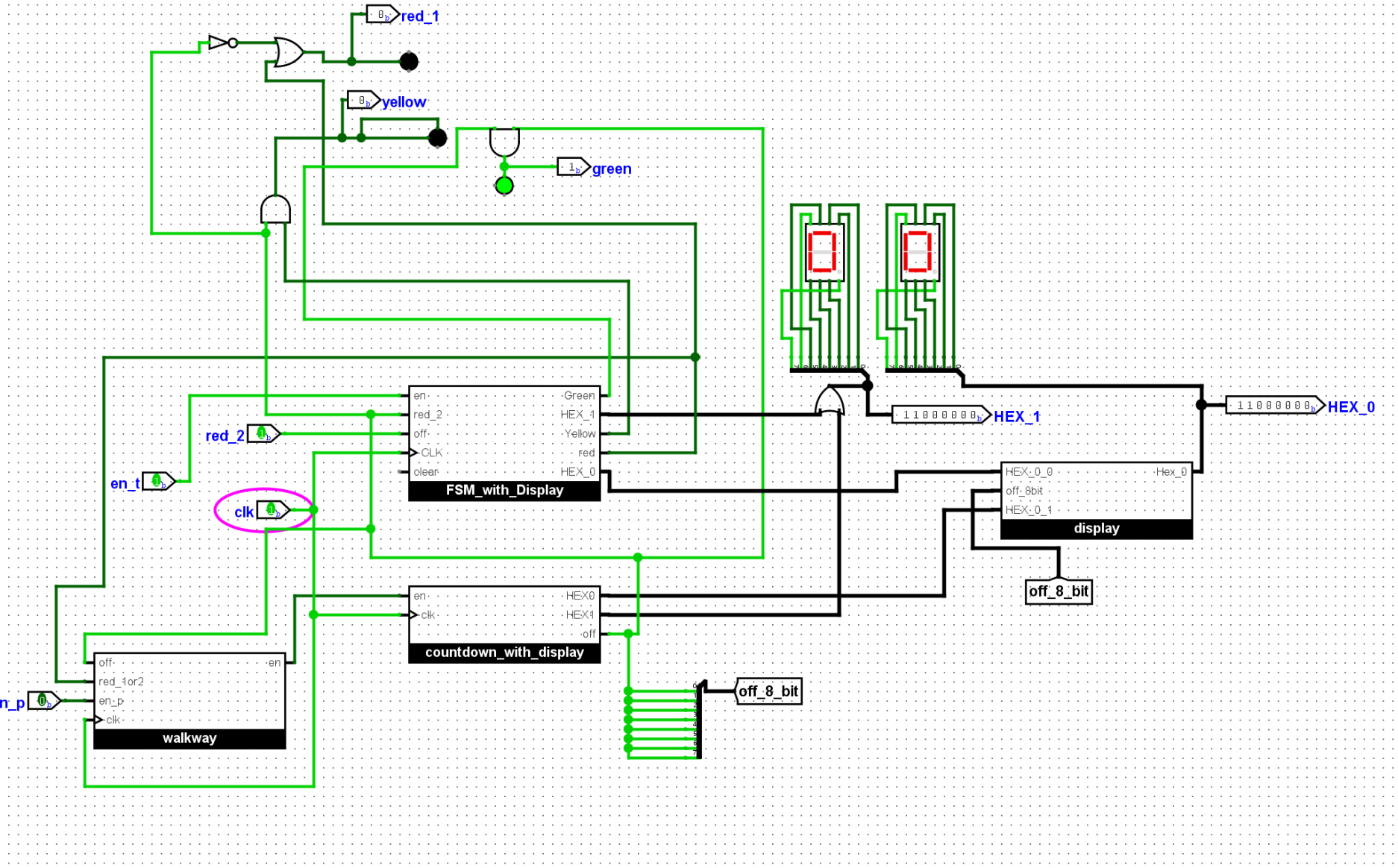

# The count for the second FSM

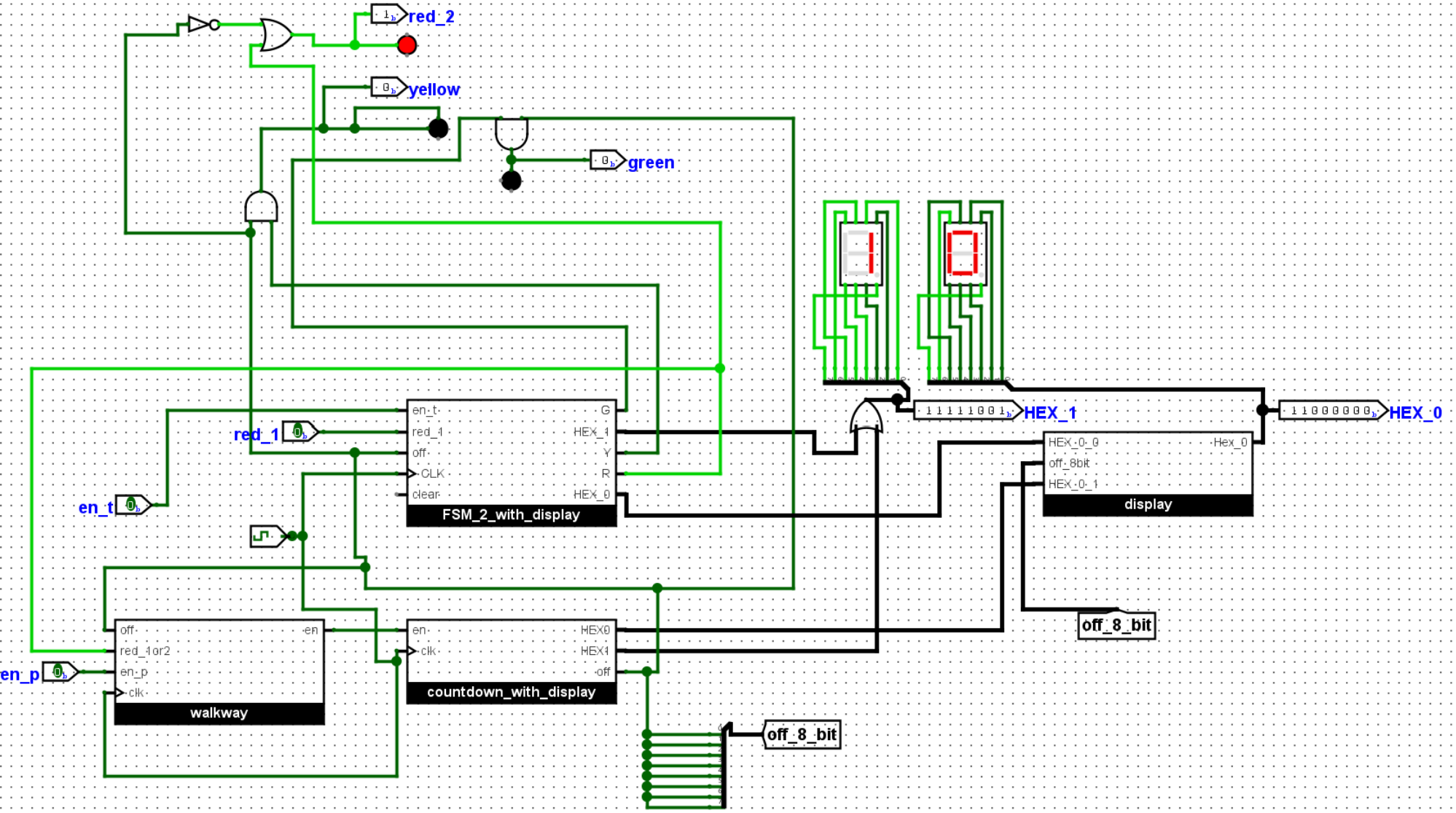
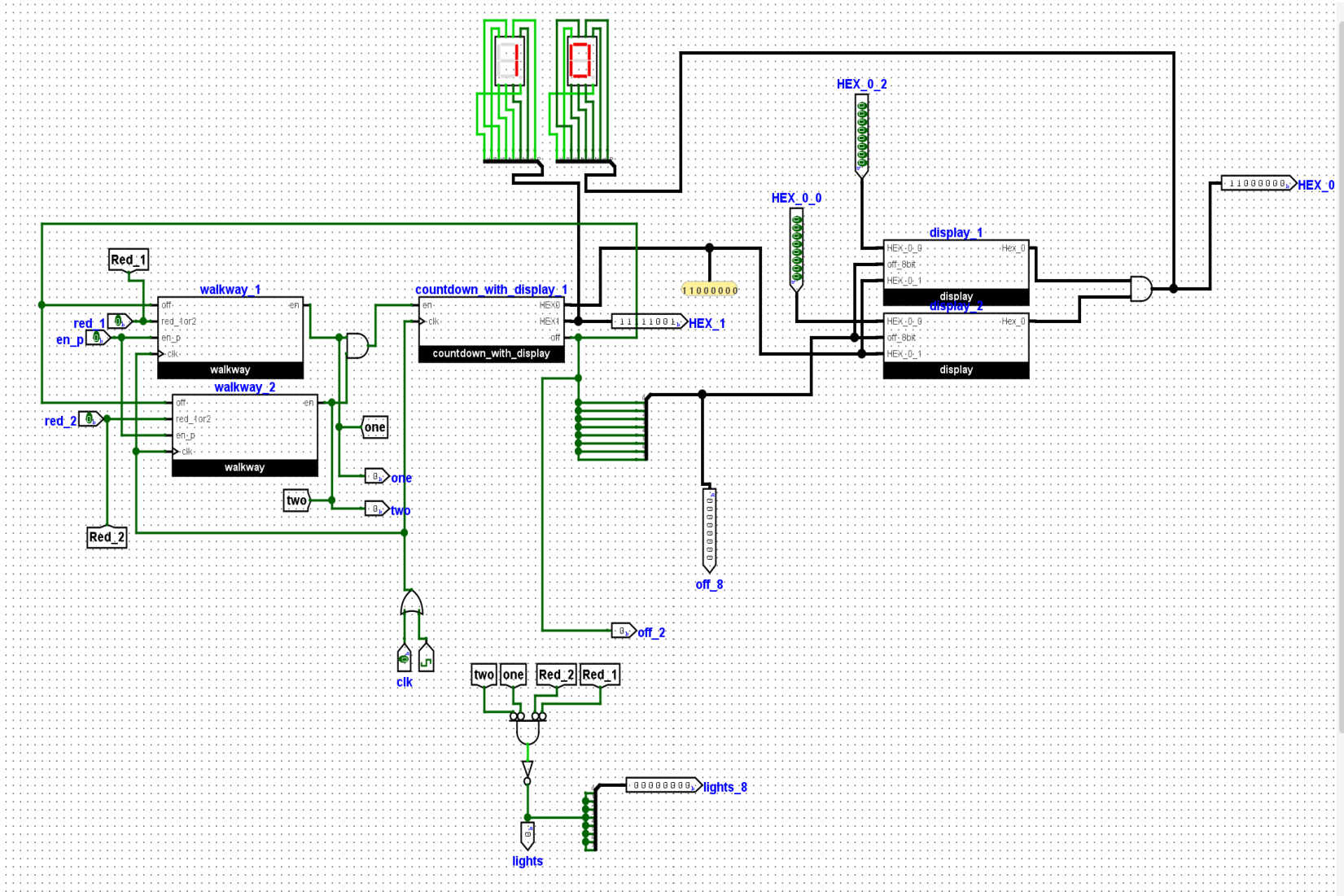
# The same idea as my walkway circuit that connects to my countdown with display but with some extra outputs and another walkway circuit



# My final design for the traffic lights and pedestrian button

